

# Assignment-F1

## Digital Logic Design

### Encoder and Decoder:

1. Design a 2-line to 4-line decoder with active low output. State how many input and output terminals your device will have with proper markings. For your design show the truth table, derive SOP output expressions, draw logic symbol/block diagram and combinational logic diagram.
2. Design a 2-line to 4-line decoder with active high output. State how many input and output terminals your device will have with proper markings. For your design show the truth table, derive SOP output expressions, draw logic symbol/block diagram and combinational logic diagram.
3. Design a 3-line to 8-line decoder with active high output. State how many input and output terminals your device will have with proper markings. For your design show the truth table, derive SOP output expressions, draw logic symbol/block diagram and combinational logic diagram.
4. Design a decimal to binary Priority encoder with the following priority sequence (1, 0, 3, 2) with 1 having highest priority and 2 with the lowest priority. State how many input and output terminals your device will have with proper markings. For your design show the truth table, derive SOP output expressions, draw logic symbol/block diagram and combinational logic diagram.
5. Design a decimal to binary Priority encoder with the following priority sequence (5, 7, 4, 6, 1, 0, 3, 2) with 5 having highest priority and 2 with the lowest priority. State how many input and output terminals your device will have with proper markings. For your design show the truth table, derive SOP output expressions, draw logic symbol/block diagram and combinational logic diagram.
6. Implement the function  $f(A,B,C,D)=(3, 5, 6,7, 9, 10, 11, 13)$ , using a 4-bit decoder and necessary gates.
7. Implement the logic function  $f(A,B,C)=AB+\bar{C}$ , using a 3-bit decoder and necessary gates.
8. Implement a Full Subtractor using a 3-bit decoder and necessary gates.

### Multiplexer and Demultiplexer:

1. Design a 4X1 Multiplexer. State how many input and output terminals your device will have with proper markings in a block diagram. For your design show the truth table, derive SOP output expressions and draw combinational logic diagram.
2. A drink dispenser machine has 7 different types of drinks that it can serve to its customer. The machine is programmed in such a way that only one of the drink is served at a time. The input switch configuration is set in the following way. 0 for Coke, 1 for Sprite, 2 for Mirinda, 3 for Coffee, 4 for Lime, 5 for Water and 6 for Mountain Dew. Design the system with the concept of Mux. State how many input and output terminals your device will have with proper markings. For your design show the truth table, derive SOP output expressions, draw logic symbol/block diagram
3. Design a 8X1 Multiplexer using 4X1 Multiplexer blocks only. State how many input and output terminals your device will have with proper markings. For your design show the truth table, derive SOP output expressions, draw logic symbol/block diagram.
4. Design a 8X1 Multiplexer using 4X1 Multiplexer and 2X1 Multiplexer blocks. State how many input and output terminals your device will have with proper markings. For your design show, the truth table, derive SOP output expressions, draw logic symbol/block diagram.
5. Implement the function  $f(A,B,C)=(3, 5, 6, 7)$  using Multiplexer. Show which pins you are choosing as selector pin in your truth table.
6. What do you understand by the term Demultiplexer?
7. Design a 1 to 2 Demultiplexer. State how many input and output terminals your device will have with proper markings in a block diagram. For your design show the truth table, derive SOP output expressions and draw combinational logic diagram.

# Assignment-F1

## Digital Logic Design

8. **Design a 1 to 4 Demultiplexer.** State how many input and output terminals your device will have with proper markings in a block diagram. For your design show the truth table, derive SOP output expressions and draw combinational logic diagram.
9. **Design a 1 to 7 Demultiplexer with 1 of 2 Demux only.** State how many input and output terminals your device will have with proper markings in a block diagram. For your design show the truth table, derive SOP output expressions.
10. **Design a 1 to 16 Demultiplexer using 1 to 2 Demultiplexer blocks only.** State how many input and output terminals your device will have with proper markings in a block diagram. For your design show the truth table, derive SOP output expressions.

Do not copy from your peers. If you do not understand anything, consult with them or me. Assignments copied will be considered obsolete. Assignment is due on quiz 4, in class. Please do not drop your assignments in my office room.