

Assignment-F2


Digital Logic Design

Sequential Logic Design:

1. What is the **basic difference** between a **combinational logic circuit** and **sequential logic circuit**?
2. What is a **latch**?
3. **Design** an active high input **S-R latch**. For the designed device, state the **truth table** and **verify it** using the **present state assumption** and **next state table** process **discussed in class**, draw **logic symbol/block diagram** and **combinational logic diagram**.
4. **Design** an active low input **S-R latch**. For the designed device, state the **truth table** and **verify it** using the **present state assumption** and **next state table** process **discussed in class**, draw **logic symbol/block diagram** and **combinational logic diagram**.
5. **Design** an active high input **gated S-R latch**. For the designed device, state the **truth table** and **verify it** using the **present state assumption** and **next state table** process **discussed in class**, draw **logic symbol/block diagram** and **combinational logic diagram**.
6. What do you **understand** by the term **flip-flop**?
7. What is the **basic difference** between an **edge-triggered device** and a **level triggered device**? **Explain with the help of diagram**.
8. **Draw the logic symbol** of a **positive edge-triggered S-R flip-flop** along with the **truth table** for it. Use the **truth table** and a **timing diagram** to **explain the operation** of the **S-R flip-flop**.
9. **Draw the logic symbol** of a **positive edge-triggered D flip-flop** along with the **truth table** for it. Use the **truth table** and a **timing diagram** to **explain the operation** of the **D flip-flop**.
10. **Draw the logic symbol and logic diagram** of a **positive edge-triggered J-K flip-flop** along with the **truth table** for it. Use the **truth table** and a **timing diagram** to **explain the operation** of the **J-K flip-flop**.
11. **Draw the logic symbol** of a **positive edge-triggered T flip-flop** along with the **truth table** for it. Use the **truth table** and a **timing diagram** to **explain the operation** of the **T flip-flop**.
12. **Draw the logic diagram** of a **Master-Slave J-K flip-flop**. **Explain the operation** of the **Master-Slave J-K flip-flop** with the help of a **timing diagram**.

Timing Diagram Problems:

 
- a) Determine the output Q and \bar{Q} of a negative edge triggered D-flip-flop if Q is initially at reset condition.




Assignment-F2

Digital Logic Design

 - b) Determine the output Q and \bar{Q} of a positive edge triggered J-K-flip-flop if Q is initially at reset condition. Here \overline{Clr} and \overline{Pre} are active low inputs which corresponds to clear and preset respectively.



 
- c) Determine the output Q and \bar{Q} of a negative edge triggered J-K-flip-flop if Q is initially at reset condition.



Assignment-F2

Digital Logic Design

 d. Determine the output Q and \bar{Q} of a Master Slave-flip-flop if Q is initially at reset condition.



Answer the timing diagrams in the question and attach it to your assignment.

Do not copy from your peers. If you do not understand anything, consult with them or me. Assignments copied will be considered obsolete. Assignment is **due on the day of quiz 5**. Please do not drop your assignments in my office room.