

# Assignment-M1

## Digital Logic Design

### Basic Logic Gate:

1. Write down the truth table, logic, logic expression and draw the logic symbol for each of the following gates

a. NOT (1 input)	b. OR	c. AND	d. NAND
e. NOR	f. XOR	g. XNOR	

with 3 inputs.

### Logic Simplification with Boolean algebra:

2. Using **Boolean algebra** and **De Morgan's Rule** where applicable, simplify the following expressions

- $AB + A(B+C) + B(B+C)$
- $A\bar{B} + A(\bar{B} + \bar{C}) + B(\bar{B} + \bar{C})$
- $[AB(C + \bar{B}\bar{D}) + \bar{A}\bar{B}]CD$
- $\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{A}\bar{B}\bar{C}$

### Building Combinational Logic Circuit and Universal Gates

3. For the following output expressions, **design the combinational logic circuits with basic logic gates (use Boolean algebra to reduce the expressions where possible).**
- For the designed logic circuits, **redraw** each of them with only **Universal NAND gates only**.
    - $ABC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}$
    - $AC + AB + \bar{B}\bar{C}$
  - For the designed logic circuits, **redraw** each of them with only **Universal NOR gates only**.
    - $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}$
    - $AC + \bar{A}\bar{B} + \bar{B}\bar{C}$

Do not copy from your peers. If you do not understand anything, consult with them or me. Assignments copied will be considered obsolete. Assignment is due on the day you sit for your 1<sup>st</sup> quiz. Keep a copy of your assignment with you for further consultation for your term exam.