

Assignment-M2

Digital Logic Design

Types of Boolean Expressions

1. **Convert** each of the following Boolean expressions to **SOP** form:

a. $(A+B)(B+C+D)$

b. $\overline{(\overline{A+B}) + C(A+D)}$

2. **Convert** the following to **Standard SOP** expressions:

a. $\overline{A}BC + A\overline{D} + \overline{B}CD$

b. $(A + \overline{B} + C)(A + B + \overline{C})$

3. **Convert** each of the following to **POS** expressions:

a. $AB+CD(\overline{A}\overline{B} + CD)$

b. $AB(\overline{B}\overline{C} + BD)$

4. **Convert** the following to **Standard POS** expressions:

a. $A+B(AC+(B+\overline{C})D)$

b. $\overline{A}\overline{B}C+\overline{A}\overline{B} + AB\overline{C}D$

5. **Develop** a **truth table** from **each of the following expressions**. (Hint: Convert them to their standard forms before you create any truth table)

a. $\overline{A}B + AB\overline{C} + \overline{A}\overline{C} + A\overline{B}C$

b. $(A + B)(A + C)(A + B + \overline{C})$

Karnaugh Map

6. **Use K-map** to find the **minimum SOP and POS expression** from the following expressions **and draw the logic gate diagrams**.

a. $AC(\overline{B} + C)$

e. $f(A,B,C,D) = \sum (3,7,8,12,15)$

b. $A+B\overline{C} + CD$

f. $f(A,B,C,D) = \prod (3,7,8,12,15)$

c. $A(B+\overline{C})(\overline{A} + C)(A+\overline{B} + C)(\overline{A} + B + \overline{C})$

g. $f(A,B,C) = \sum (0,2,5,7)$

d. $\overline{A}B(\overline{C}\overline{D} + \overline{C}D) + AB(\overline{C}\overline{D} + \overline{C}D) + A\overline{B}\overline{C}D$

h. $f(A,B,C) = \prod (1,2,6,7)$

Don't Care Condition:

7. The following is a **truth-table** of a **combinational logic circuit**. With inputs **A, B, C, D** and output **F**.

Fill-up a K-MAP out of the truth-table.

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	X
0	0	1	1	X
0	1	0	0	X
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	X
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	X
1	1	1	0	0
1	1	1	1	1

a. **Derive the simplified expression using K-map (without using don't care values).**

b. **Derive the simplified expression using K-map (using don't care values).**

c. **Using your results in parts a and b, explain the importance of using don't care terms.**

Assignment-M2

Digital Logic Design

8. Consider the given expression:

$$F(A,B,C,D) = \sum (3,7,8,12,15)$$

$$d(A,B,C,D) = (1,5,9,10,11)$$

where **d(A,B,C,D)** represents the don't care conditions.

Fill-up a K-MAP with the above data.

1. Derive the simplified SOP expression using **K-map** (without using don't care values).
2. Derive the simplified expression using **K-map** (using don't care values).
3. Using your results in parts 1 and 2, **explain the importance of using don't care terms**

9. Consider the given expression:

$$F(A,B,C,D) = \prod (1,5,9,10,11)$$

$$d(A,B,C,D) = (3,7,8,12,15)$$

where **d(A,B,C,D)** represents the don't care conditions.

Fill-up a K-MAP with the above data.

1. Derive the simplified expression POS using **K-map** (without using don't care values).
2. Derive the simplified expression using **K-map** (using don't care values).
3. Using your results in parts 1 and 2, **explain the importance of using don't care terms**

Do not copy from your peers. If you do not understand anything, consult with them or me. Assignments copied will be considered obsolete. Assignment is **due on quiz-2 day, before you sit for your QUIZ-2**. Keep a copy of your assignment with you for further consultation for your term exam.