

9-1 BASIC SHIFT REGISTER FUNCTIONS


Shift registers consist of arrangements of flip-flops and are important in applications involving the storage and transfer of data in a digital system. A register, unlike a counter, has no specified sequence of states, except in certain very specialized applications. A register, in general, is used solely for storing and shifting data (1s and 0s) entered into it from an external source and typically possesses no characteristic internal sequence of states.

After completing this section, you should be able to

- Explain how a flip-flop stores a data bit
- Define the storage capacity of a shift register
- Describe the shift capability of a register


A register can consist of one or more flip-flops used to store and shift data.

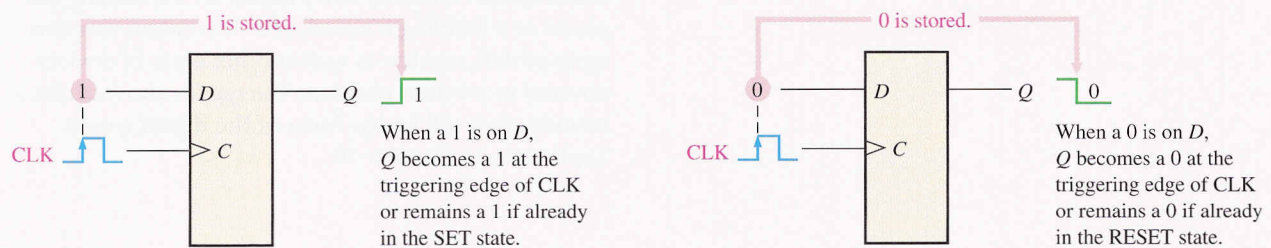A **register** is a digital circuit with two basic functions: data storage and data movement. The storage capability of a register makes it an important type of memory device. Figure 9-1 illustrates the concept of storing a 1 or a 0 in a D flip-flop. A 1 is applied to



▲ FIGURE 9-1

The flip-flop as a storage element.

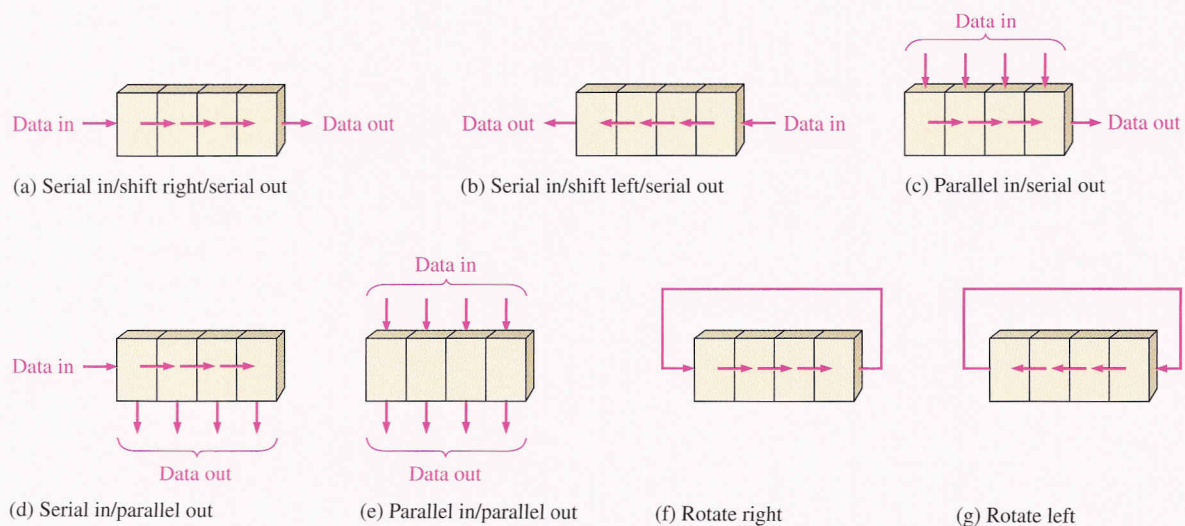

▲ FIGURE 9-2

Basic data movement in shift registers. (Four bits are used for illustration. The bits move in the direction of the arrows.)

the data input as shown, and a clock pulse is applied that stores the 1 by *setting* the flip-flop. When the 1 on the input is removed, the flip-flop remains in the SET state, thereby storing the 1. A similar procedure applies to the storage of a 0 by *resetting* the flip-flop, as also illustrated in Figure 9-1.

The *storage capacity* of a register is the total number of bits (1s and 0s) of digital data it can retain. Each **stage** (flip-flop) in a shift register represents one bit of storage capacity; therefore, the number of stages in a register determines its storage capacity.

The **shift** capability of a register permits the movement of data from stage to stage within the register or into or out of the register upon application of clock pulses. Figure 9-2 illustrates the types of data movement in shift registers. The block represents any arbitrary 4-bit register, and the arrows indicate the direction of data movement.

SECTION 9-1 REVIEW

Answers are at the end of the chapter.

1. Generally, what is the difference between a counter and a shift register?
2. What two principal functions are performed by a shift register?


9-2 SERIAL IN/SERIAL OUT SHIFT REGISTERS

The serial in/serial out shift register accepts data serially—that is, one bit at a time on a single line. It produces the stored information on its output also in serial form.

After completing this section, you should be able to

- Explain how data bits are serially entered into a shift register
- Describe how data bits are shifted through the register
- Explain how data bits are serially taken out of a shift register
- Develop and analyze timing diagrams for serial in/serial out registers

 Let's first look at the serial entry of data into a typical shift register. Figure 9-3 shows a 4-bit device implemented with D flip-flops. With four stages, this register can store up to four bits of data.



▲ FIGURE 9-3

Serial in/serial out shift register.


Figure 9-4 illustrates entry of the four bits 1010 into the register, beginning with the right-most bit. The register is initially clear. The 0 is put onto the data input line, making $D = 0$ for FF0. When the first clock pulse is applied, FF0 is reset, thus storing the 0.

Next the second bit, which is a 1, is applied to the data input, making $D = 1$ for FF0 and $D = 0$ for FF1 because the D input of FF1 is connected to the Q_0 output. When the second

COMPUTER NOTE



Frequently, it is necessary to *clear* an internal register in a computer. For example, a register may be cleared prior to an arithmetic or other operation. One way that registers in a computer are cleared is using software to subtract the contents of the register from itself. The result of course, will always be zero. For example, a computer instruction that performs this operation is SUB AL,AL. With this instruction, the register named AL is cleared.

 ▲ **FIGURE 9-4**


Four bits (1010) being entered serially into the register.

clock pulse occurs, the 1 on the data input is shifted into FF0, causing FF0 to set; and the 0 that was in FF0 is shifted into FF1.

The third bit, a 0, is now put onto the data-input line, and a clock pulse is applied. The 0 is entered into FF0, the 1 stored in FF0 is shifted into FF1, and the 0 stored in FF1 is shifted into FF2.

The last bit, a 1, is now applied to the data input, and a clock pulse is applied. This time the 1 is entered into FF0, the 0 stored in FF0 is shifted into FF1, the 1 stored in FF1 is shifted into FF2, and the 0 stored in FF2 is shifted into FF3. This completes the serial entry of the four bits into the shift register, where they can be stored for any length of time as long as the flip-flops have dc power.

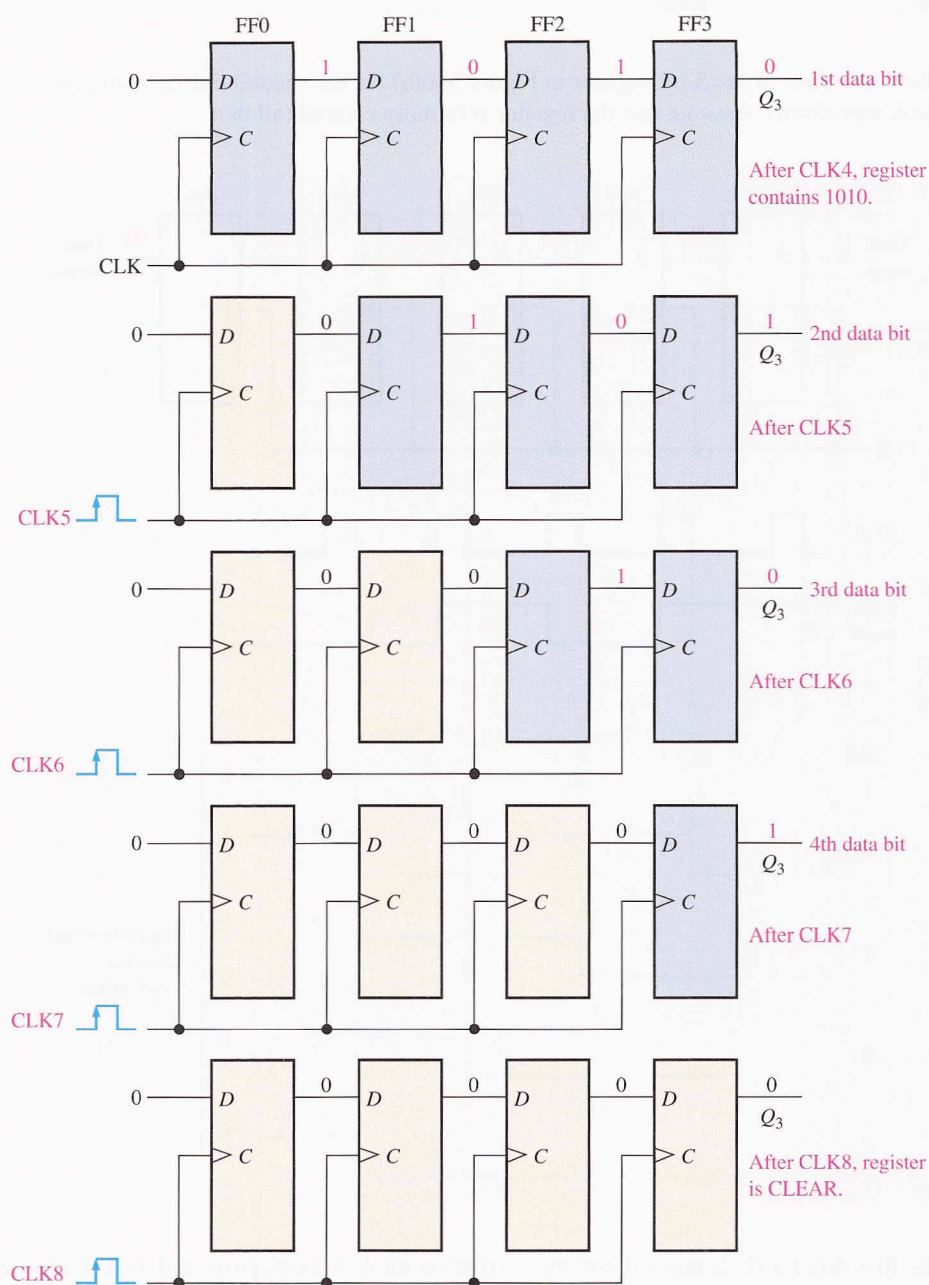For serial data, one bit at a time is transferred.



▲ **FIGURE 9-5**

Four bits (1010) being serially shifted out of the register and replaced by all zeros.


If you want to get the data out of the register, the bits must be shifted out serially and taken off the Q_3 output, as Figure 9-5 illustrates. After CLK4 in the data-entry operation just described, the right-most bit, 0, appears on the Q_3 output. When clock pulse CLK5 is applied, the second bit appears on the Q_3 output. Clock pulse CLK6 shifts the third bit to the output, and CLK7 shifts the fourth bit to the output. While the original four bits are being shifted out, more bits can be shifted in. All zeros are shown being shifted in.

EXAMPLE 9-1

Show the states of the 5-bit register in Figure 9-6(a) for the specified data input and clock waveforms. Assume that the register is initially cleared (all 0s).

FIGURE 9-6

Open file F09-06 to verify operation.

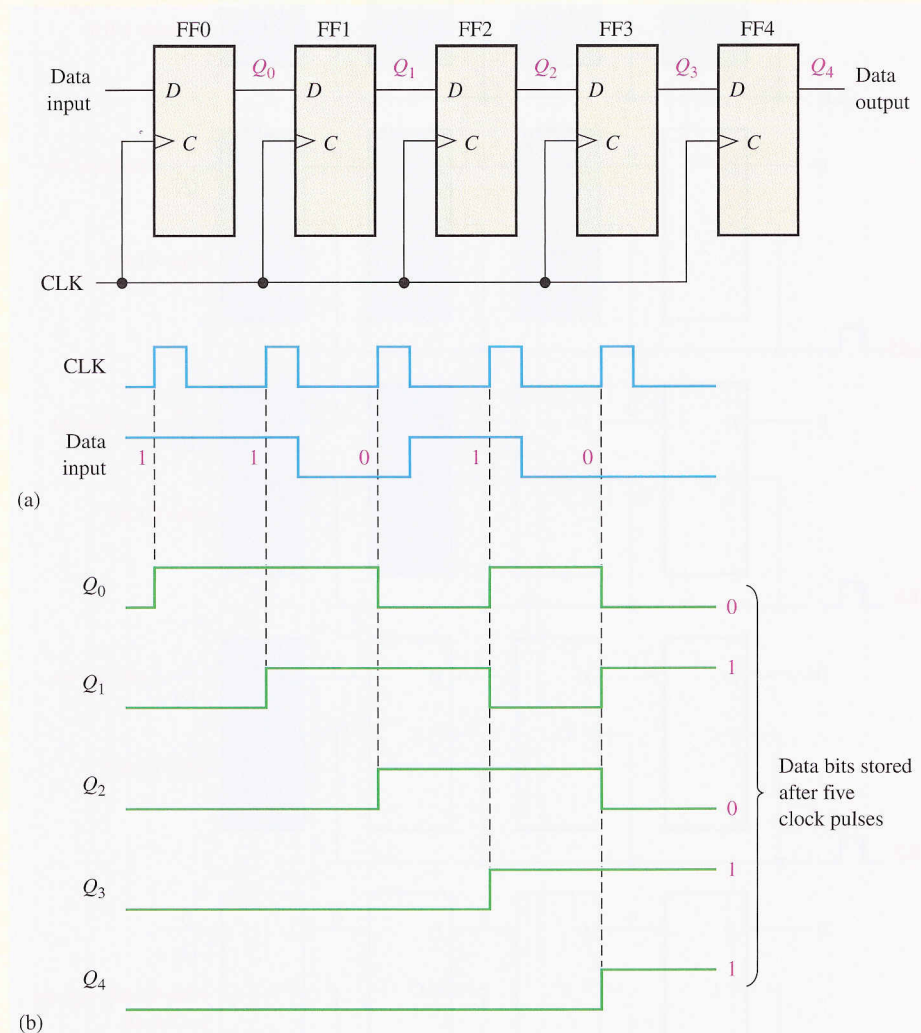

Solution The first data bit (1) is entered into the register on the first clock pulse and then shifted from left to right as the remaining bits are entered and shifted. The register contains $Q_4Q_3Q_2Q_1Q_0 = 11010$ after five clock pulses. See Figure 9-6(b).


Related Problem * Show the states of the register if the data input is inverted. The register is initially cleared.

*Answers are at the end of the chapter.

A traditional logic block symbol for an 8-bit serial in/serial out shift register is shown in Figure 9-7. The “SRG 8” designation indicates a shift register (SRG) with an 8-bit capacity.

FIGURE 9-7

Logic symbol for an 8-bit serial in/serial out shift register.

 

SECTION 9-2 REVIEW

1. Develop the logic diagram for the shift register in Figure 9-3, using J-K flip-flops to replace the D flip-flops.
2. How many clock pulses are required to enter a byte of data serially into an 8-bit shift register?


9-3 SERIAL IN/PARALLEL OUT SHIFT REGISTERS

Data bits are entered serially (right-most bit first) into this type of register in the same manner as discussed in Section 9-2. The difference is the way in which the data bits are taken out of the register; in the parallel output register, the output of each stage is available. Once the data are stored, each bit appears on its respective output line, and all bits are available simultaneously, rather than on a bit-by-bit basis as with the serial output.

After completing this section, you should be able to

- Explain how data bits are taken out of a shift register in parallel
- Compare serial output to parallel output
- Discuss the 74HC164 8-bit shift register
- Develop and analyze timing diagrams for serial in/parallel out registers

Figure 9-8 shows a 4-bit serial in/parallel out shift register and its logic block symbol.

 

▲ FIGURE 9-8

A serial in/parallel out shift register.


EXAMPLE 9-2

Show the states of the 4-bit register (SRG 4) for the data input and clock waveforms in Figure 9-9(a). The register initially contains all 1s.

Solution The register contains 0110 after four clock pulses. See Figure 9-9(b).

Related Problem If the data input remains 0 after the fourth clock pulse, what is the state of the register after three additional clock pulses?

 A sample timing diagram for the 74HC164 is shown in Figure 9–11. Notice that the serial input data on input A are shifted into and through the register after input B goes HIGH.



▲ **FIGURE 9–11**

Sample timing diagram for a 74HC164 shift register.

SECTION 9–3 REVIEW

1. The bit sequence 1101 is serially entered (right-most bit first) into a 4-bit parallel out shift register that is initially clear. What are the Q outputs after two clock pulses?
2. How can a serial in/parallel out register be used as a serial in/serial out register?

9–4 PARALLEL IN/SERIAL OUT SHIFT REGISTERS

For a register with parallel data inputs, the bits are entered simultaneously into their respective stages on parallel lines rather than on a bit-by-bit basis on one line as with serial data inputs. The serial output is the same as described in Section 9–2, once the data are completely stored in the register.